 


## Objectives

40 Marks

1. The address from which the data is read, is provided by \_\_\_\_\_.
  - Depends on circuitry
  - None of given options
  - RAM
  - **Microprocessor**
2. The best state assignment tends to \_\_\_\_\_.
  - Maximizes the number of state variables that don't change in a group of related states
  - **Minimizes the number of state variables that don't change in a group of related states**
  - Minimize the equivalent states
  - None of given options
3. The total amount of memory that is supported by any digital system depends upon \_\_\_\_\_.
  - The organization of memory
  - The structure of memory
  - The size of decoding unit
  - **The size of the address bus of the microprocessor**
4. The expression  $F=A+B+C$  describes the operation of three bits \_\_\_\_\_ Gate.
  - **OR**
  - AND
  - NOT
  - NAND
5. The output of this circuit is always \_\_\_\_\_.



- 1
  - 0
  - **A**
  - $\bar{A}$
6. A Nibble consists of \_\_\_\_\_ bits
    - 2
    - **4**

- 8
- 16

7. In asynchronous transmission when the transmission line is idle, \_\_\_\_\_

- It is set to logic low
- It is set to logic high
- Remains in previous state
- State of transmission line is not used to start transmission

8. The \_\_\_\_\_ input overrides the \_\_\_\_\_ input

- Asynchronous, synchronous
- Synchronous, asynchronous
- Preset input (PRE), Clear input (CLR)
- Clear input (CLR), Preset input (PRE)

9. In a sequential circuit the next state is determined by \_\_\_\_\_ and \_\_\_\_\_

- State variable, current state
- Current state, flip-flop output
- **Current state and external input**
- Input and clock signal applied

10. A 8-bit serial in / parallel out shift register contains the value "8", \_\_\_\_\_ clock signal(s) will be required to shift the value completely out of the register.

- 1
- 2
- 4
- **8**

11. The 4-bit 2's complement representation of "+5" is \_\_\_\_\_

- 1010
- 1110
- 1011
- **0101**

12. Stack is an acronym for \_\_\_\_\_

- FIFO memory
- **LIFO memory**
- Flash Memory
- Bust Flash Memory

13. FIFO is an acronym for \_\_\_\_\_

- **First In, First Out**
- Fly in, Fly Out
- Fast in, Fast Out
- None of given options

14. DRAM stands for \_\_\_\_\_

➤ **Dynamic RAM**

- Data RAM
- Demoduler RAM
- None of given options

15. The alternate solution for a DE multiplexer-register combination circuit is \_\_\_\_\_

- Parallel in / Serial out shift register
- Serial in / Parallel out shift register
- Parallel in / Parallel out shift register
- Serial in / Serial Out shift register

16. In a state diagram, the transition from a current state to the next state is determined by

➤ **Current state and the inputs**

- Current state and outputs
- Previous state and inputs
- Previous state and outputs

17. \_\_\_\_\_ Counters as the name indicates are not triggered simultaneously.

- Asynchronous
- Synchronous
- Positive-Edge triggered
- Negative-Edge triggered

18. " $A + B = B + A$ " is \_\_\_\_\_

- DE Morgan's Law
- Distributive Law
- **Commutative Law**
- Associative Law

19. For a positive edge-triggered J-K flip-flop with both J and K HIGH, the outputs will \_\_\_\_\_ if the clock goes HIGH.

- Toggle
- Set
- Reset
- Not change

## Subjective

5 Questions Each have 3 Marks.

Q # 41:

Two state assignments are given in the table below. Identify which state assignment is best and why?

States	State assignment 1	State assignment 2
A	00	00
B	01	01
C	11	10
D	10	11

Q # 42:

Determine the SOP Expression for Karnaugh map given below

		C	
		0	1
AB	00	1	
	01		1
	11	1	1
	10		

Q # 43:

Draw the Symbol of Operational Amplifier (Op-Amp).

Q # 44:

Write the Difference b/w Counter and Shift register?

Q # 55:

What are the modes in which a D-Latch Operations?

## 5 Questions Each have 5 marks:

**Q # 46:**


Give Function Table of 8 Input Multiplexer using two 4 Input Multiplexer.

**Q # 47:**

Two Input Combination for which the gated S-R Latch maintain its previous state?

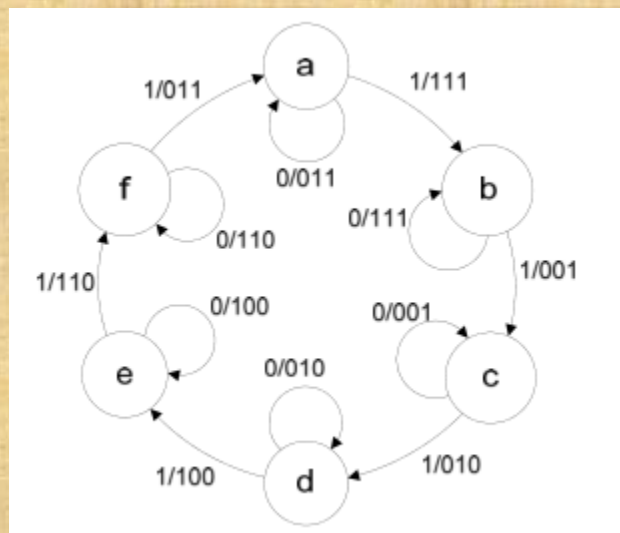**Q # 48:**

This is State diagram of a Mealy Machine. Draw the Next State Table of Mealy Machine and showing Present State, Next State, Input and Output.



**Q # 49:**

Write The Test Vector Definition of 3-bit Up/Down Counter.

**Q # 50:**

Write the answer as Yes or No in Column C.

Column A	Column B	Column C
SRAM	One-Transistor Cell	
EEPROM	High Density	
ROM	In-System Write ability	
DRAM	Non-Volatile	