

Marks											
-------	--	--	--	--	--	--	--	--	--	--	--

Question No: 1 (Marks: 1) - Please choose one

Superposition theorem can be applied only to circuit having

- ▶ Non-linear
- ▶ Passive
- ▶ Linear bilateral
- ▶ Resistive

Question No: 2 (Marks: 1) - Please choose one

The output of a half wave rectifier is suitable only

- ▶ Running car diodes
- ▶ Charging
- ▶ Diode rating
- ▶ Purity of power output

Question No: 3 (Marks: 1) - Please choose one

While calculating R_{th} current sources in the circuit are

- ▶ Replaced by
- ▶ Replaced indirect voltage
- ▶ Replaced by short
- ▶ Replaced DC voltage

Question No: 4 (Marks: 1) - Please choose one

In parallel circuits all components

- ▶ have the same value

- ▶ have same potential
- ▶ carry the same
- ▶ be switched ON & OFF simultaneously

Question No: 5 (Marks: 1) - Please choose one

The clipping level is primarily determined by

- ▶ shape of the input
- ▶ value of the resistor
- ▶ battery
- ▶ knee voltage of the

Question No: 6 (Marks: 1) - Please choose one

The depletion region of a P-N junction is

- ▶ During the manufacturing
- ▶ When forward bias is applied to it
- ▶ Under reverse bias
- ▶ When its temperature is

Question No: 7 (Marks: 1) - Please choose one

The dc load line of a transistor can be drawn if we know its cut off and

- ▶ active
- ▶ saturation

- ▶ quiescent
- ▶ None of them

Question No: 8 (Marks: 1) - Please choose one

The filter is simply a capacitor connected in ----- with the load

- ▶ series
- ▶ parallel
- ▶ we can use it in series as well as in parallel
- ▶ none of

Question No: 9 (Marks: 1) - Please choose one

Zener diode is operated in the Region

- ▶ cut-off
- ▶ forward
- ▶ breakdow
- ▶ saturation

Question No: 10 (Marks: 1) - Please choose one

A tunnel diode is always biased

- ▶ By dc source
- ▶ In the reverse direction

- ▶ In the middle of its negative resistance region

- ▶ None of them

Question No: 11 (Marks: 15)

Use nodal analysis to find out the power supplied by current source in the network given Identify and label each node otherwise you will lose your marks. Write each step of the to get maximum marks and also mention the units of each derived

Question No: 12 (Marks: 10)

Find V_o in the network given below using **Thevenin's** . Show each step of calculation otherwise you will lose your marks. Draw and label the diagram of each step and also mention the units of each derived

Question No: 13 (Marks: 10)

Find I_o in the network given below using **Norton's** . Show each step of calculation otherwise you will lose your marks. Draw and label the diagram of each step and also mention the units of each derived

Question No: 14 (Marks: 15)

(a) Measurement on the circuit below produces labeled voltages as indicated. Find the value β for the given circuit. **Marks=6**

(b) For the circuit shown in the figure below, find the emitter, base, and collector voltages currents. Use $\beta = 32$, but assume $|V_{BE}| = 0.7V$ independent of current level. **Marks: 9**

www.vustuff.com

